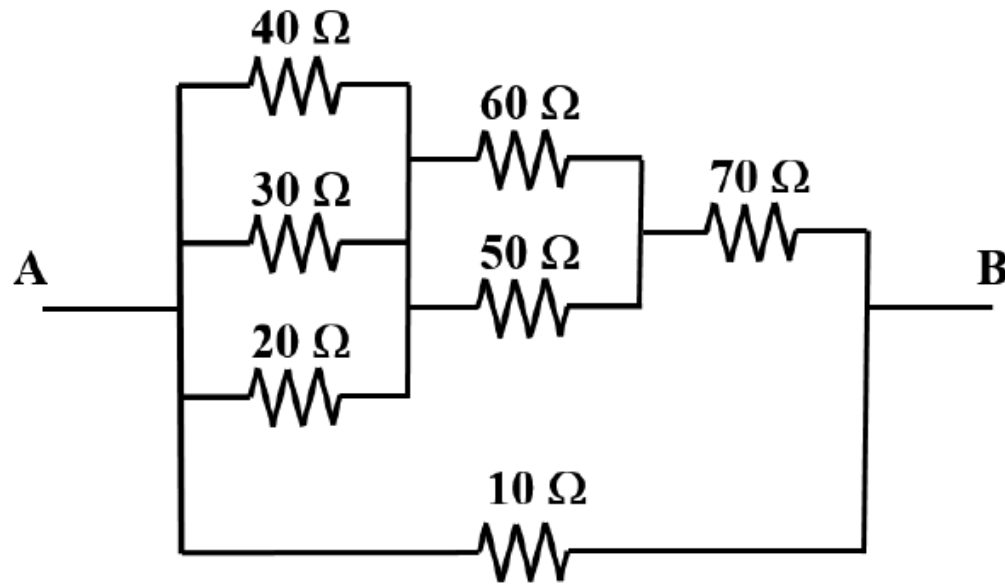


CG1111A: Engineering Principles & Practice I

Revision Practice Questions for Quiz #1



Q1




For the resistor network shown in the figure above, what is the equivalent resistance R_{AB} between the terminals A and B?

- (A) 9.14 Ω
- (B) 10.94 Ω
- (C) 106.5 Ω
- (D) 116.5 Ω

Ans: A

Q2

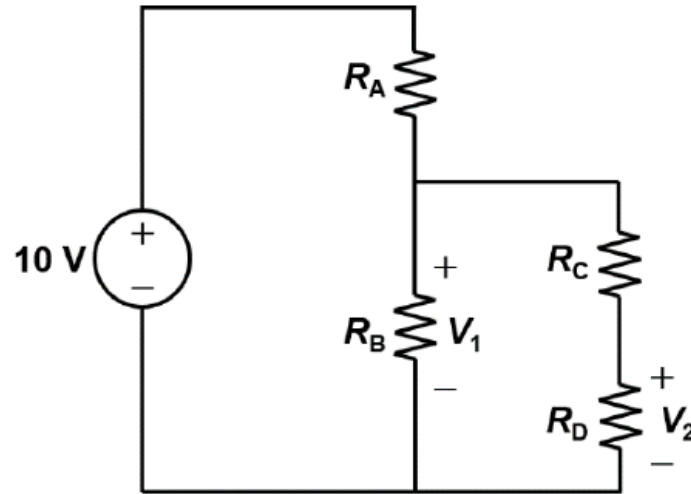


Benedict, who'd just learnt about the voltage divider principle, is excited about applying it to build a circuit shown in the figure above. He wishes to obtain $V_1 = 6\text{ V}$, and $V_2 = 2\text{ V}$. However, he does not realize that he cannot apply the principle directly to R_A and R_B , as resistors R_C and R_D have a “loading effect”. Which one of the following sets of resistor values would allow him to get V_1 and V_2 to be closest to his desired voltages of 6 V and 2 V, respectively?

	R_A	R_B	R_C	R_D
(A)	$40\ \Omega$	$60\ \Omega$	$400\ \Omega$	$200\ \Omega$
(B)	$40\ \Omega$	$60\ \Omega$	$4000\ \Omega$	$2000\ \Omega$
(C)	$400\ \Omega$	$600\ \Omega$	$40\ \Omega$	$20\ \Omega$
(D)	$4000\ \Omega$	$6000\ \Omega$	$40\ \Omega$	$20\ \Omega$

Ans: B

Q3

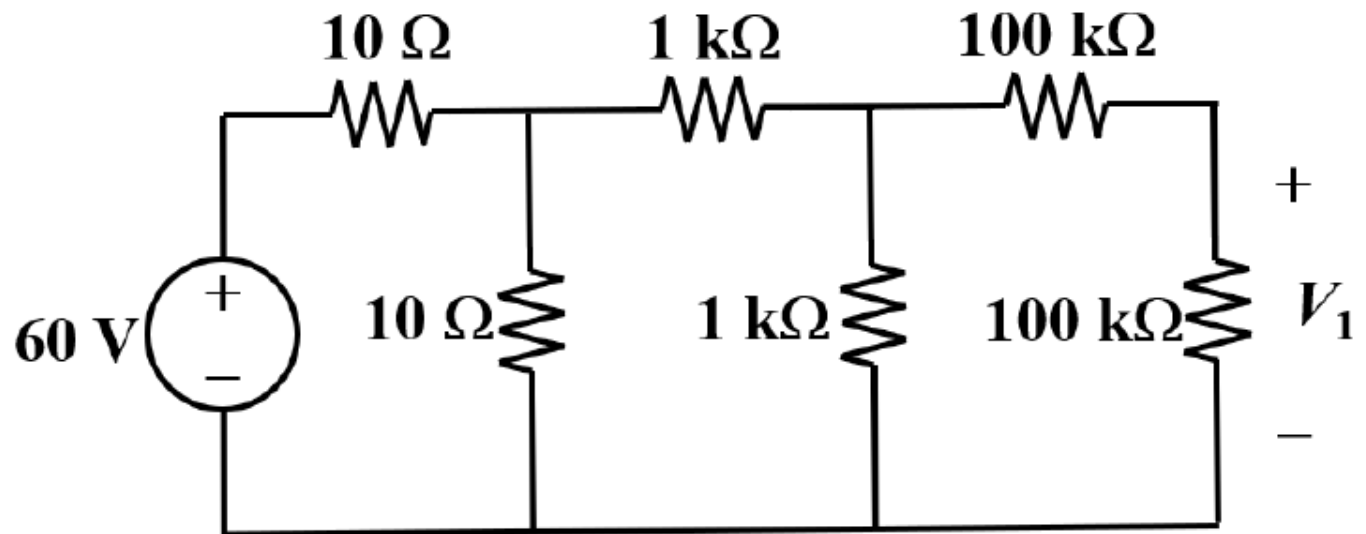


For the circuit shown in the figure above, what is the voltage V_1 ?

- A: 5.4 V
- B: 7.5 V
- C: 15.0 V
- D: 30.0 V

Ans: B (most common mistakes: C and D)

Q4

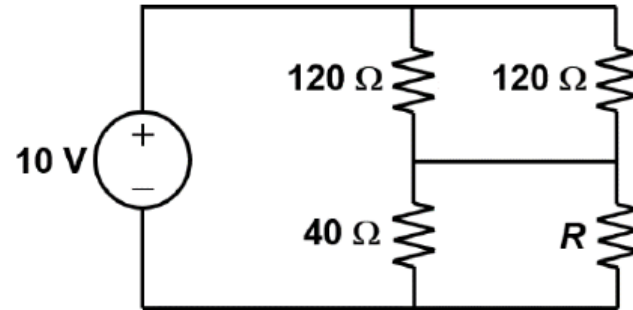


What is the value of R that will result in a current of 0.1 A passing through R ?
(Hint: Use Thevenin equivalent circuit)

- (A) 56 Ω
- (B) 24 Ω
- (C) 40 Ω
- (D) 16 Ω

Ans: D

Q5

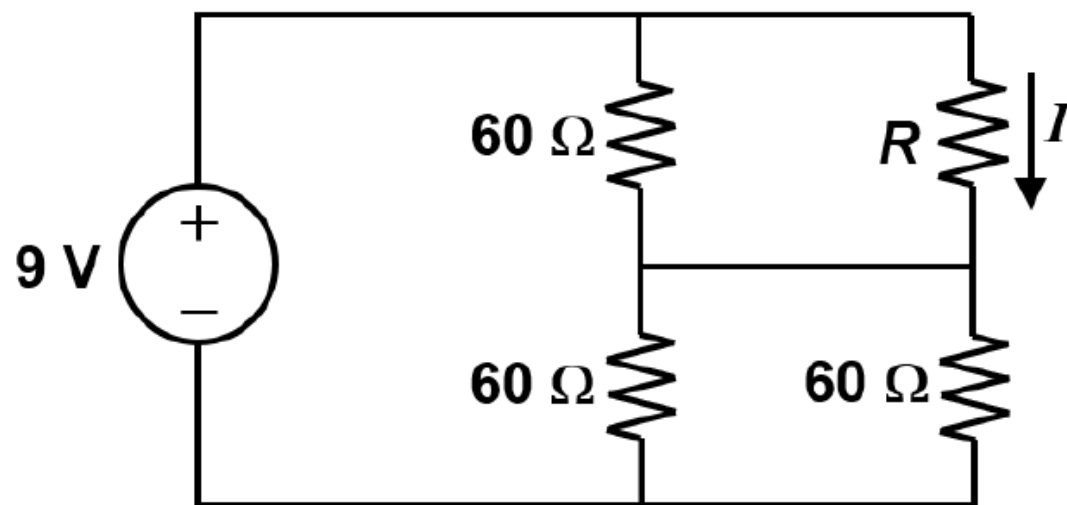


What is the value of R that will result in a current of $I = 0.15$ A passing through R ?
(Hint: Use Thevenin equivalent circuit)

- A: 60 Ω
- B: 40 Ω
- C: 30 Ω
- D: 20 Ω

Ans: D (most common mistake: B)

Q6

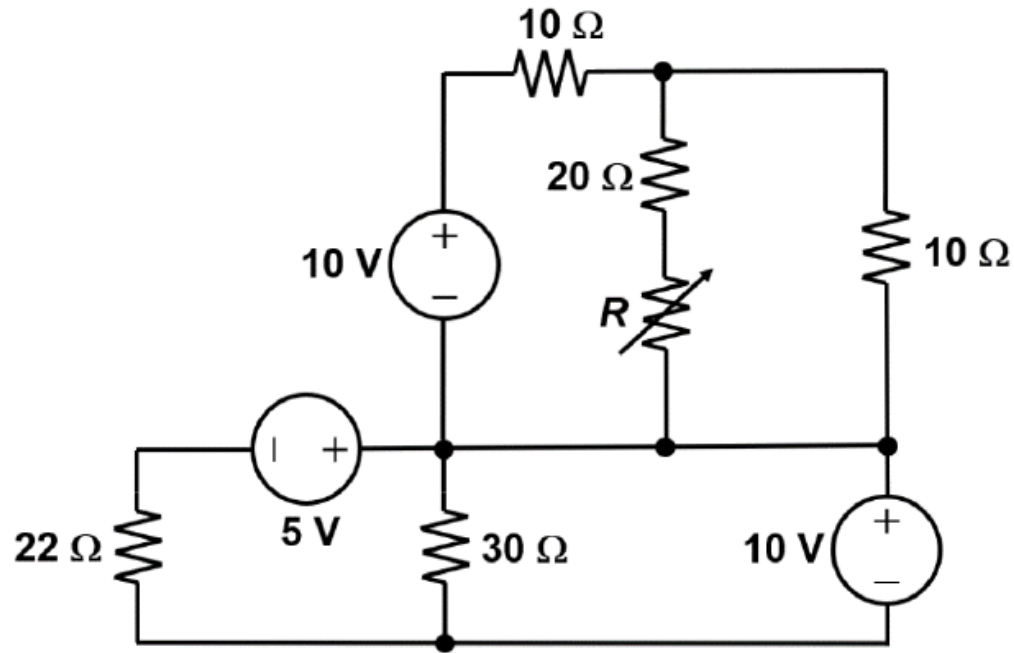


What is this maximum power that can be utilized by the load R ?

- (A) 0.25 W
- (B) 1 W
- (C) 1.56 W
- (D) 6.25 W

Ans: A

Q7

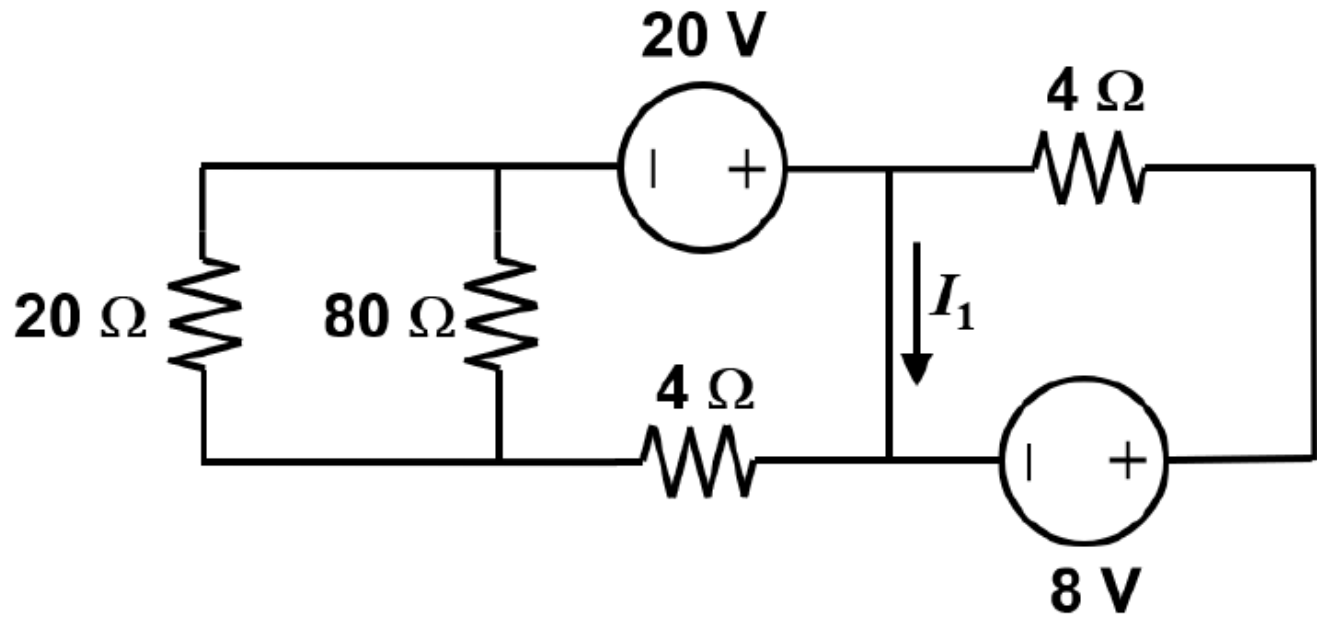


For the circuit shown in the figure above, what is the value of current I_1 ?

- A: 0 A
- B: 1 A
- C: 2 A
- D: 3 A

Ans: D (most common mistake: B)

Q8

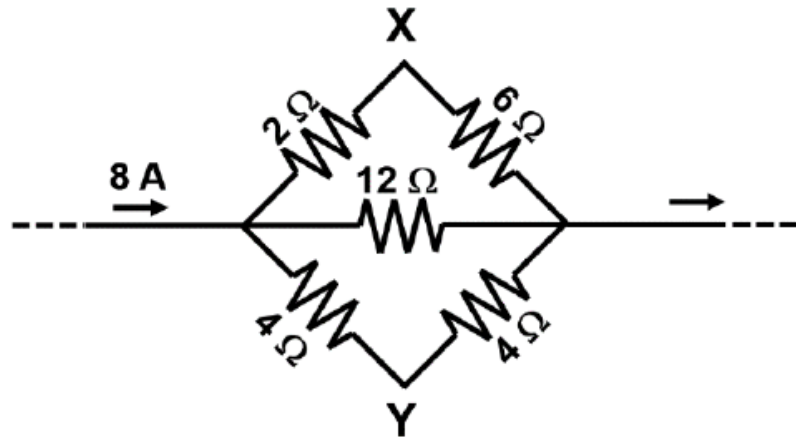


A current of 8 A flows through a resistor network as shown in the figure above. The voltage difference V_{XY} (given by $V_X - V_Y$) is

- (A) 12 V
- (B) 6 V
- (C) 4.57 V
- (D) 11.4 V

Ans: B

Q9

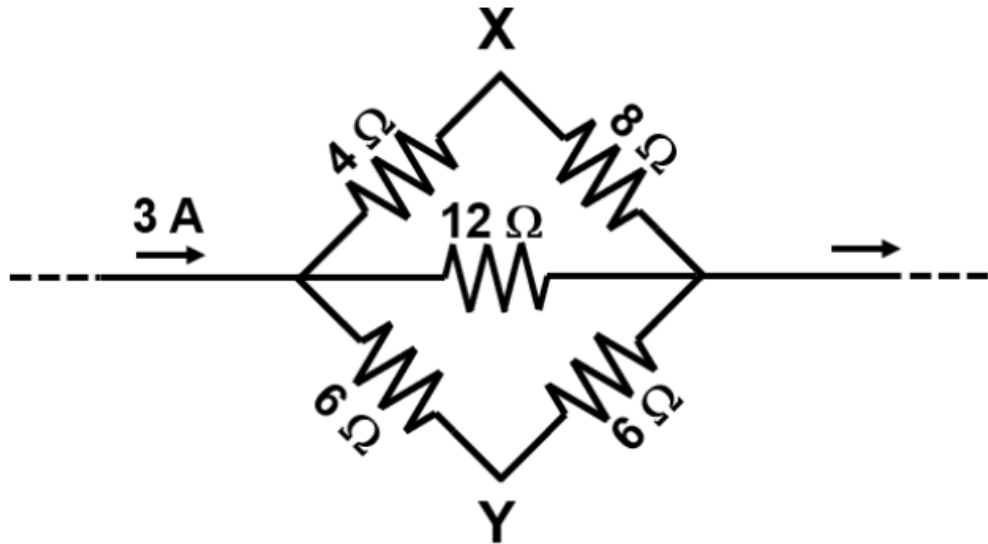


A current of 3 A flows through a resistor network as shown in the figure above. The voltage difference V_{XY} (given by $V_X - V_Y$) is

- A: 2 V
- B: -2 V
- C: 5 V
- D: 8 V

Ans: A (most common mistake: B)

Q10

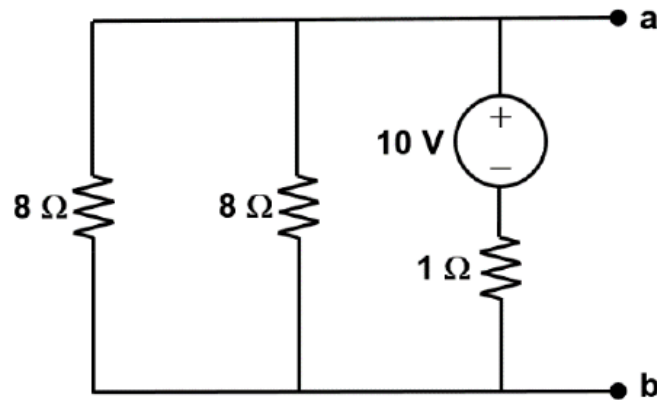


Suppose a load resistance R_L is to be placed across the nodes **a** and **b** in the circuit above, so as to draw maximum power. What is this maximum power that can be utilized by the load R_L ?

- (A) 10 W
- (B) 20 W
- (C) 40 W
- (D) 80 W

Ans: B

Q11

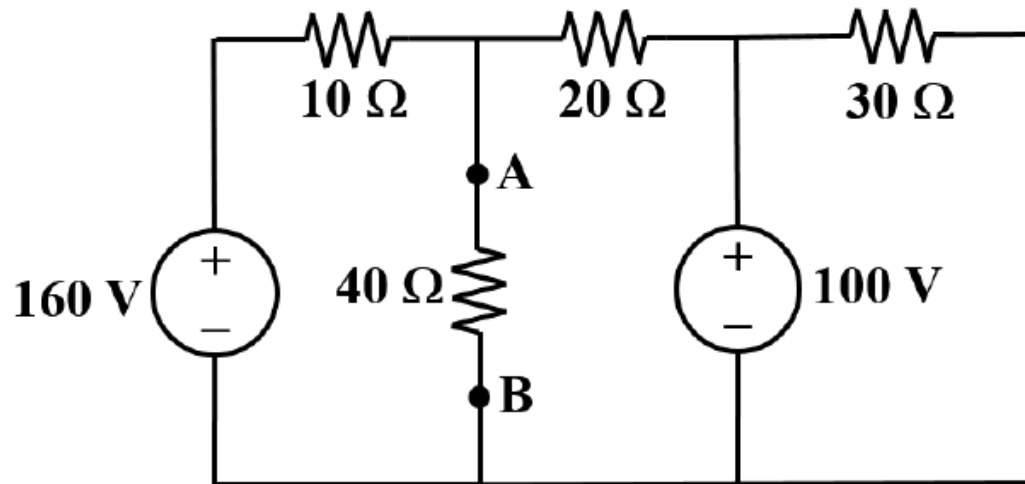


For the circuit shown in the figure above, what is the Thevenin equivalent circuit as seen by the 40 Ω resistor (i.e., between nodes A and B)?

- (A) $V_T = 120 \text{ V}, R_T = 6.67 \text{ } \Omega$
- (B) $V_T = 140 \text{ V}, R_T = 6.67 \text{ } \Omega$
- (C) $V_T = 120 \text{ V}, R_T = 5.45 \text{ } \Omega$
- (D) $V_T = 140 \text{ V}, R_T = 5.45 \text{ } \Omega$

Ans: B

Q12

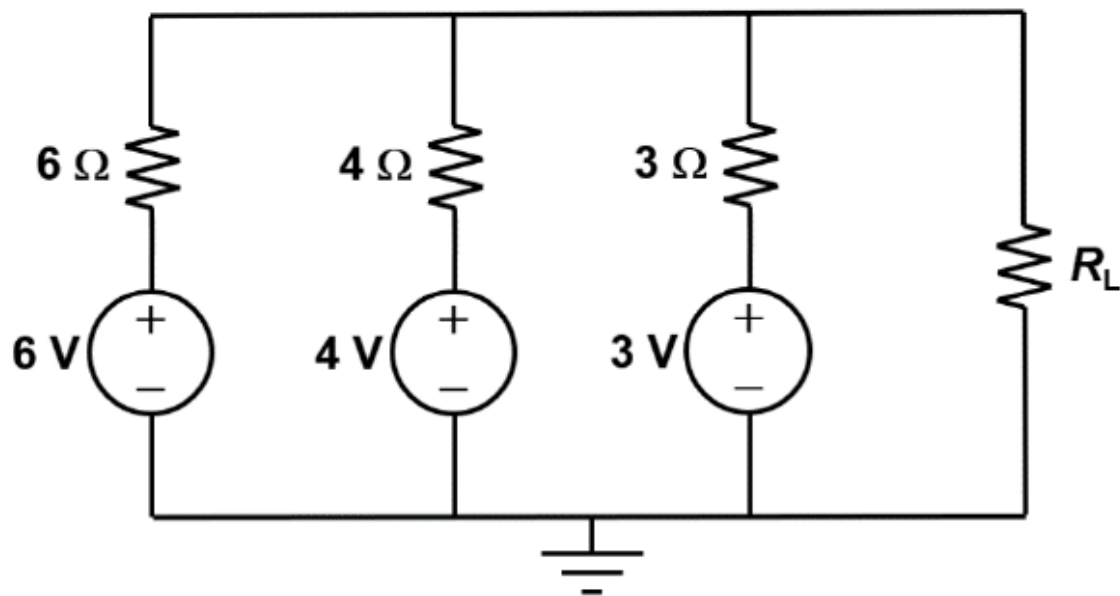


For the circuit shown in the figure above, what is the Thevenin equivalent circuit's *Thevenin voltage* as seen by the load R_L ?

- A: 4 V
- B: 2.4 V
- C: 4.56 V
- D: 4.28 V

Ans: A (most common mistake: uniform for the other 3 options... random guesses!)

Q13

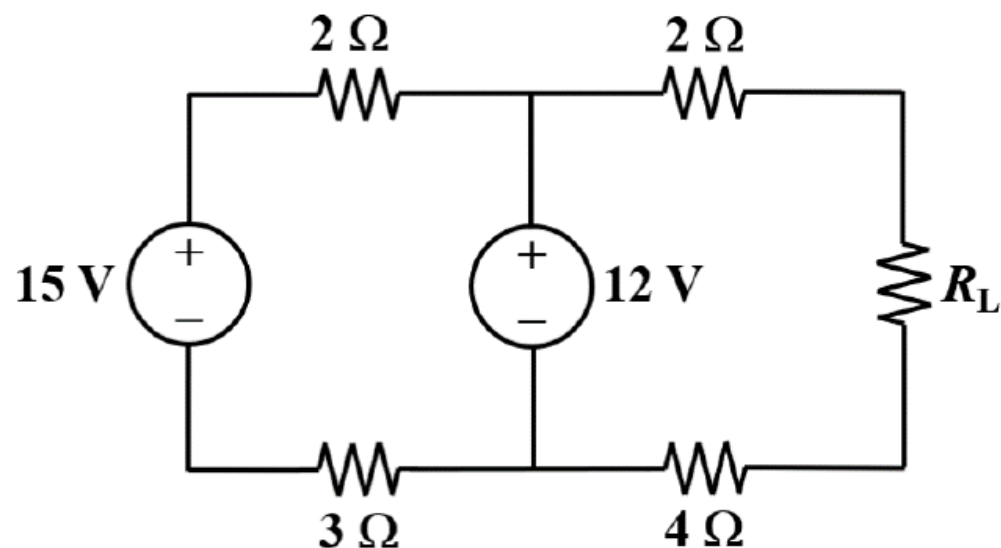


For the circuit shown in the figure above, what is the Thevenin equivalent circuit's *Thevenin resistance* as seen by the load R_L ?

- A: 6 Ω
- B: 1.33 Ω
- C: 7.2 Ω
- D: 2.53 Ω

Ans: A (most common mistake: D)

Q14

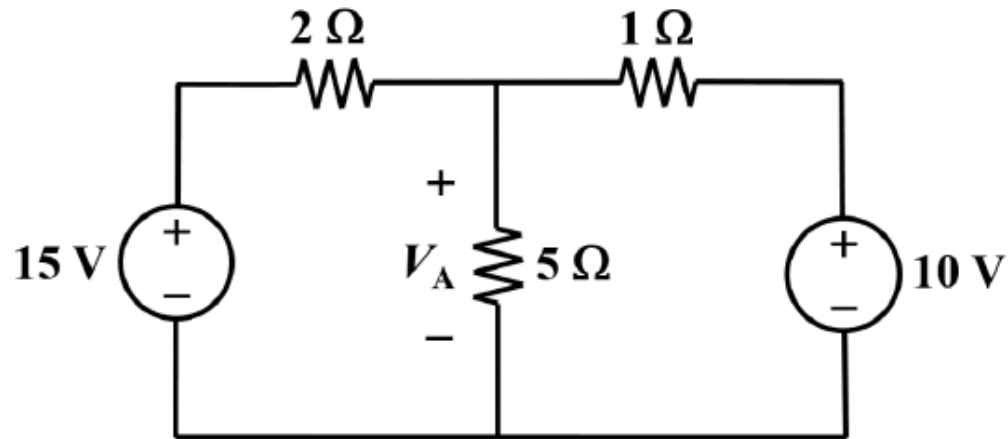


For the circuit shown in the figure above, what is the voltage V_A ?

- (A) 12.1 V
- (B) 11.7 V
- (C) 11.3 V
- (D) 10.3 V

Ans: D

Q15

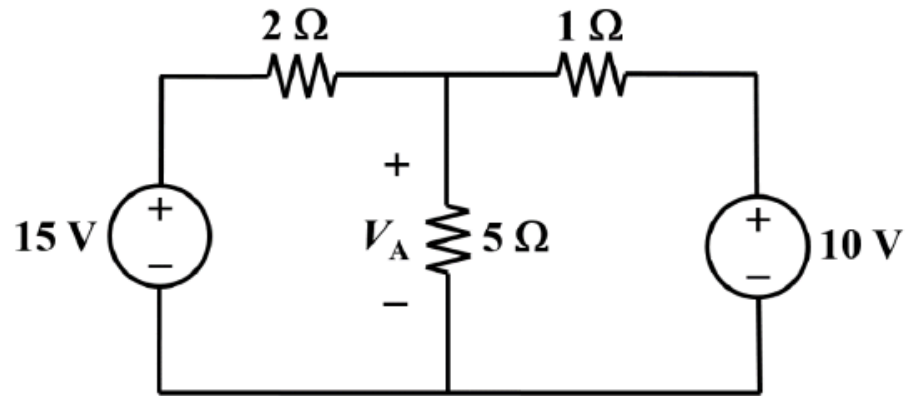


For the circuit shown in the figure above, the 10 V voltage source is

- (A) supplying a power of about 28 W.
- (B) consuming a power of about 21 W.
- (C) consuming a power of about 3 W.
- (D) consuming a power of about 13 W.

Ans: C

Q16

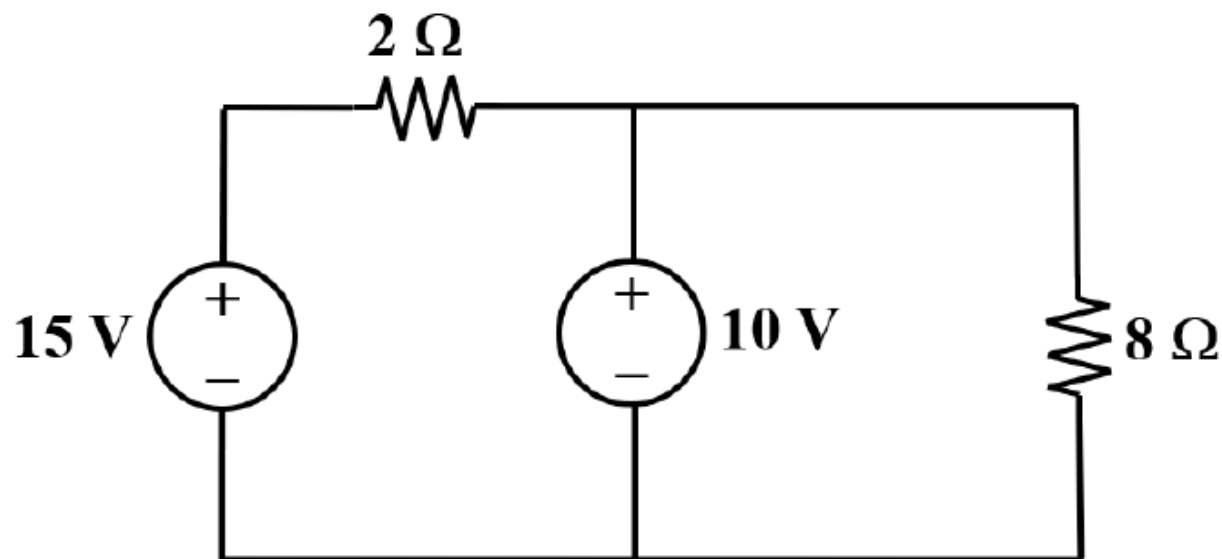


For the circuit shown in the figure above, the 10 V voltage source is

- A: consuming a power of 12.5 W.
- B: supplying a power of 12.5 W.
- C: supplying a power of 37.5 W.
- D: consuming a power of 25 W.

Ans: A (most common mistake: D)

Q17

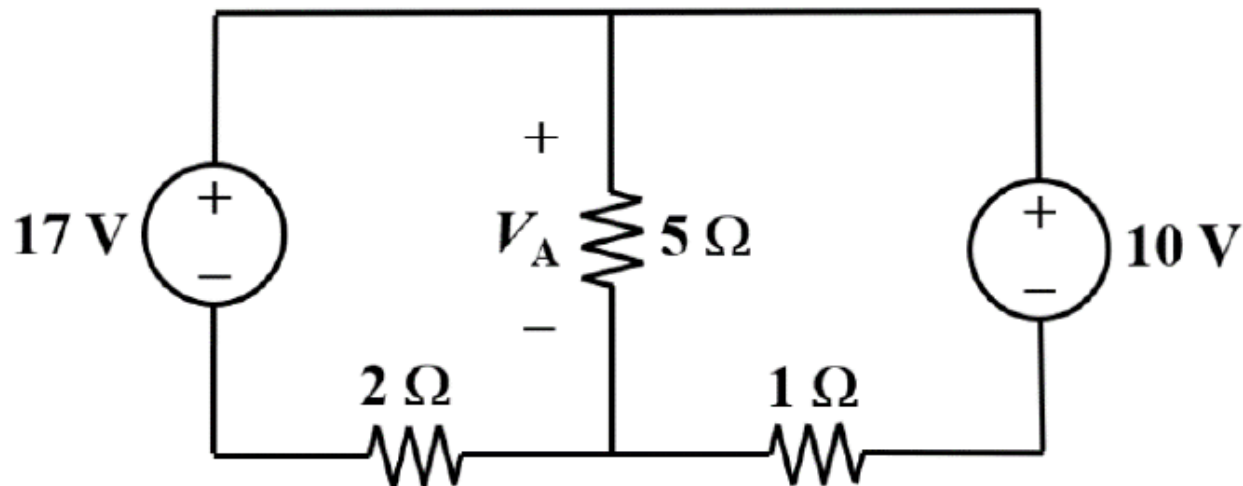


For the circuit shown in the figure above, what is the voltage V_A ?

- A: 10.9 V
- B: 11.9 V
- C: 12.3 V
- D: 12.7 V

Ans: A (most common mistake: C)

Q18

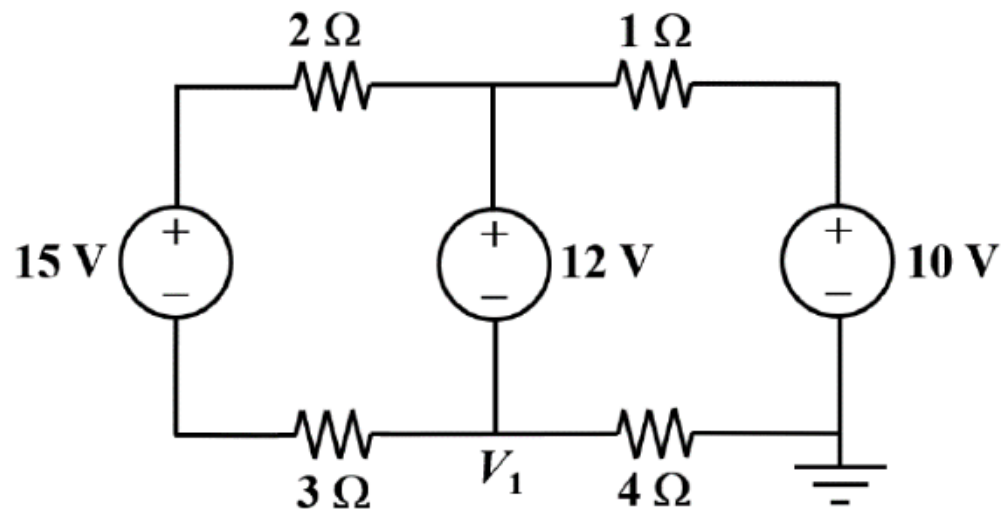


For the circuit shown in the figure above, what is the voltage V_1 with respect to ground?

- (A) 3.4 V
- (B) -3.4 V
- (C) 1.6 V
- (D) -1.6 V

Ans: D

Q19

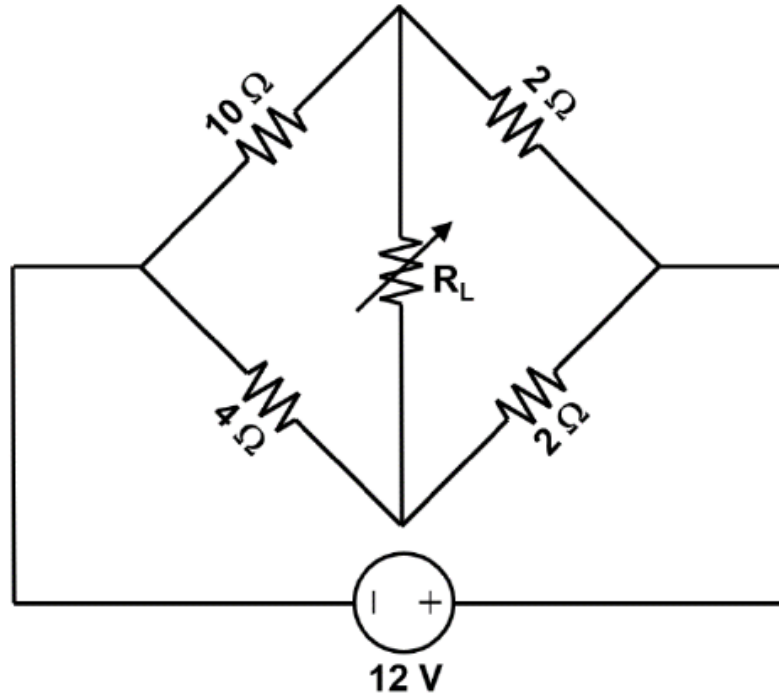


What is the maximum power that can be utilized by the variable load R_L ?

- A: 333 mW
- B: 1.33 W
- C: 4 W
- D: 259 mW

Ans: A (most common mistake: B)

Q20

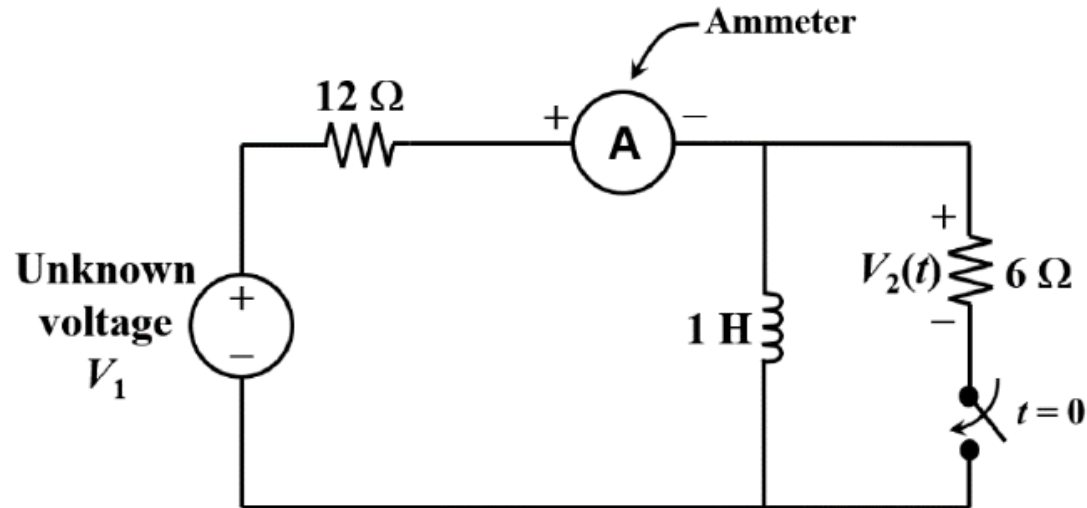


For the circuit shown in the figure above, the switch has been opened for a long time, and the current measured by the ammeter was $1\ \text{A}$ before time $t = 0$. At time $t = 0$, the switch is closed. What would be the voltage $V_2(t)$ at time $t = 0^+\ \text{s}$?

- (A) $0\ \text{V}$
- (B) $-6\ \text{V}$
- (C) $4\ \text{V}$
- (D) $6\ \text{V}$

Ans: A

Q21

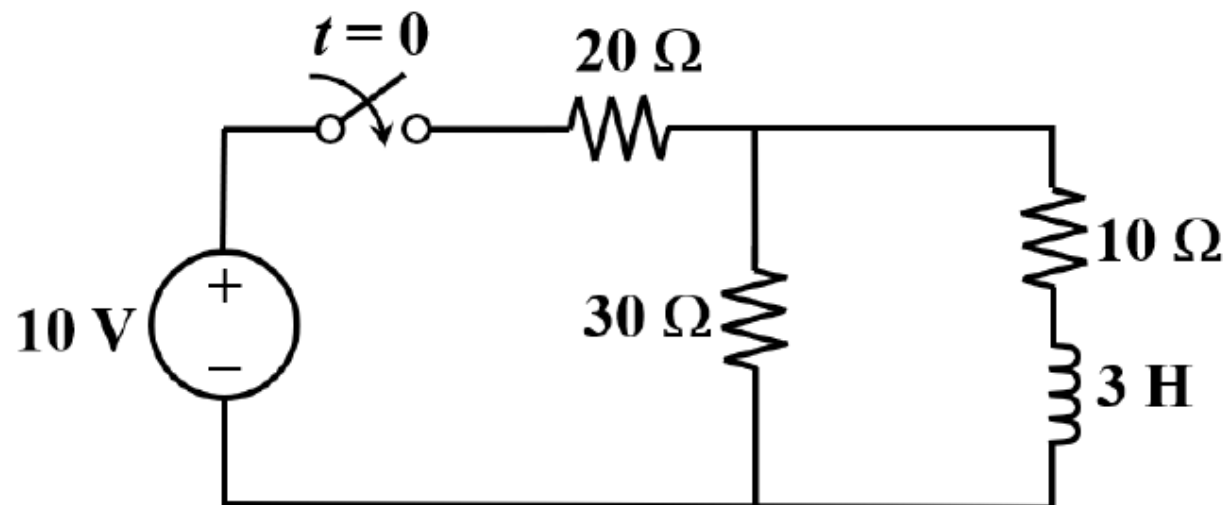


What is the time constant (τ) for the inductor's current after $t = 0$?

- A: 136 ms
- B: 109 ms
- C: 50 ms
- D: 81.8 ms

Ans: A (most common mistake: B)

Q22

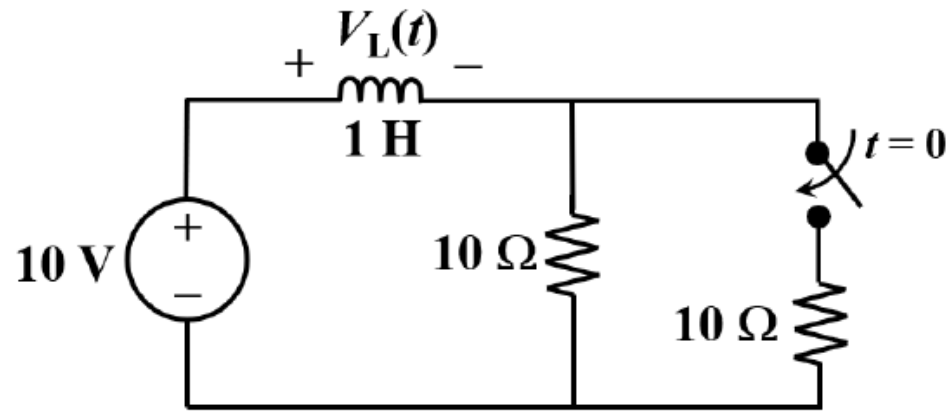


In the circuit shown in the figure above, the switch was initially OPEN for a long time. At time $t = 0$, the switch is closed. What is the inductor's voltage $V_L(t)$ at time $t = 0.2$ s?

- (A) 8.16 V
- (B) 1.84 V
- (C) 6.32 V
- (D) 3.68 V

Ans: B

Q23

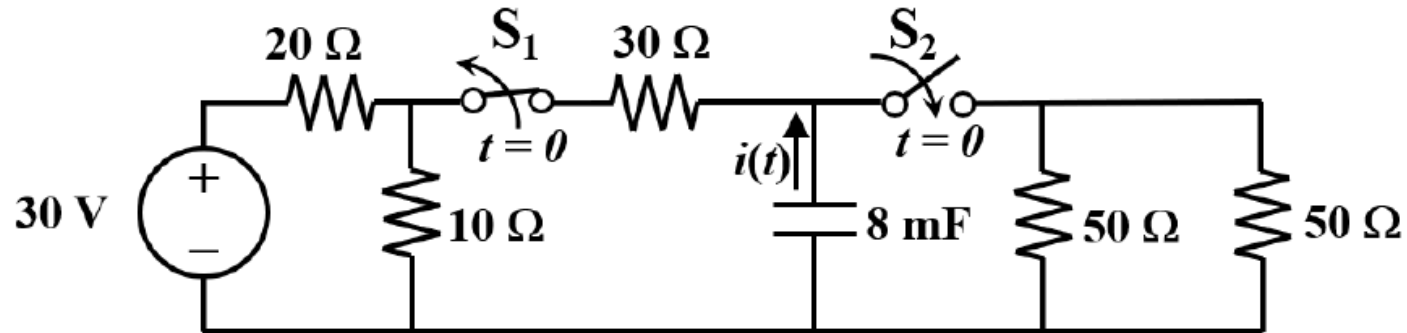


In the circuit shown in the figure above, switch S_1 was CLOSED and switch S_2 was OPEN for a long time before time $t = 0$. At time $t = 0$, both switches are flipped (i.e., S_1 becomes OPEN, and S_2 becomes CLOSED). What is the capacitor's current $i(t)$ at time $t = 0.2$ second?

- (A) 0.147 A
- (B) 0.253 A
- (C) 3.68 A
- (D) 73.6 mA

Ans: A

Q24

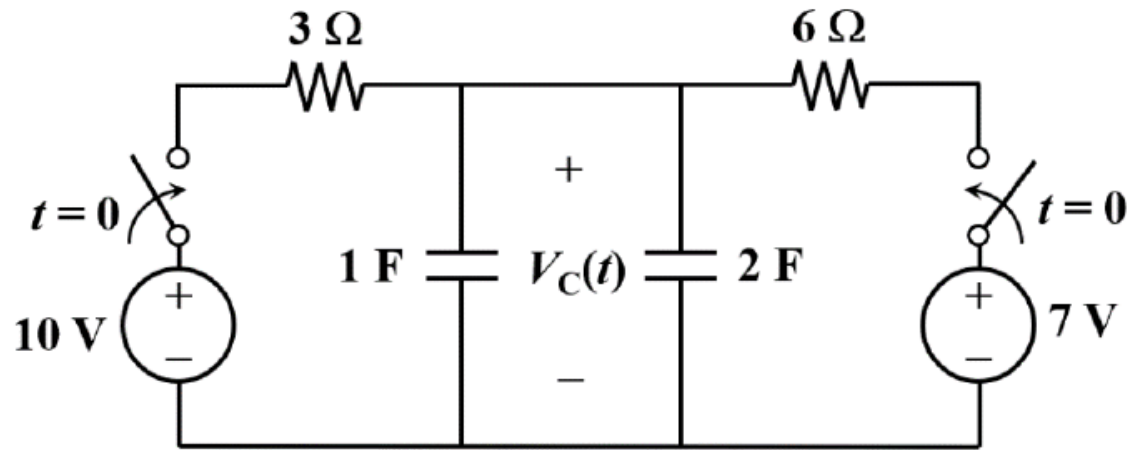


In the circuit shown in the figure above, the two capacitors were fully discharged initially. At time $t = 0$, both the switches are closed simultaneously. How long does it take for the voltage $V_c(t)$ to reach 5 V?

- A: 4.9 s
- B: 7.4 s
- C: 22.1 s
- D: 1.6 s

Ans: A (most common mistake: B and D)

Q25

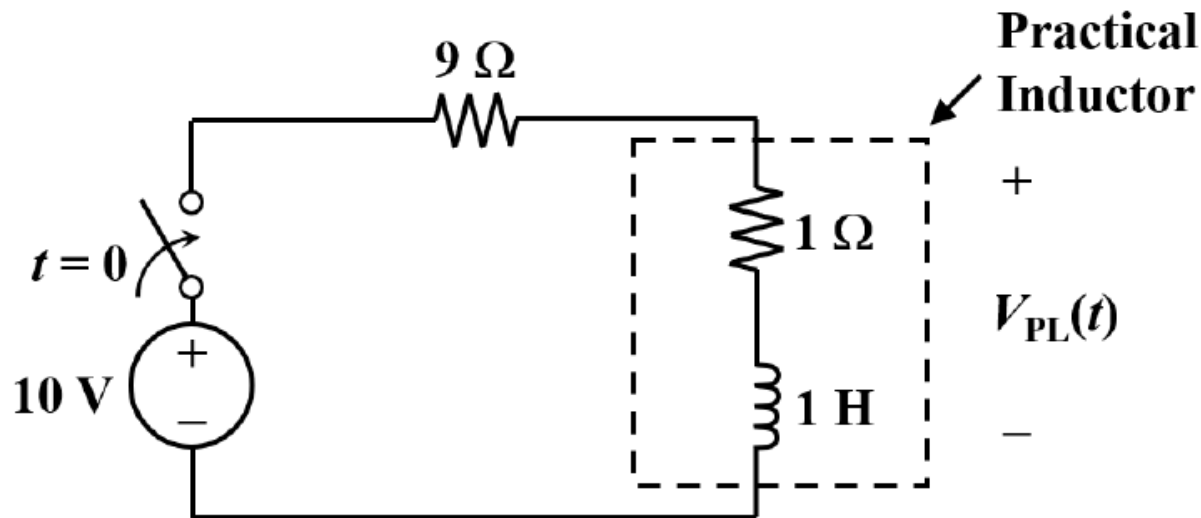


In the circuit shown in the figure above, the switch was initially OPEN for a long time. At time $t = 0$, the switch is closed. What is the practical inductor's voltage $V_{PL}(t)$ at time $t = 0.1$ s?

- A: 4.31 V
- B: 0.63 V
- C: 5.69 V
- D: 1.00 V

Ans: A (most common mistake: B)

Q26

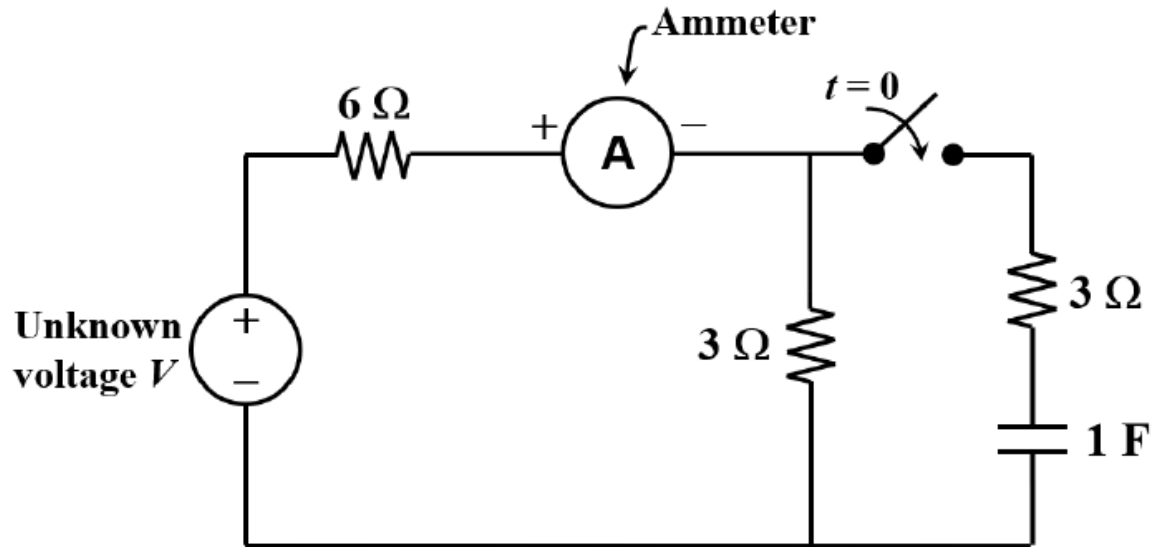


In the circuit shown in the figure above, the capacitor was fully discharged initially, and the current measured by the ammeter was 2 A before time $t = 0$. At time $t = 0$, the switch is closed. What would be the ammeter's reading at time $t = 5\ \text{s}$?

- A: 2.15 A
- B: 2.00 A
- C: 3.00 A
- D: 2.37 A

Ans: A (most common mistake: D)

Q27

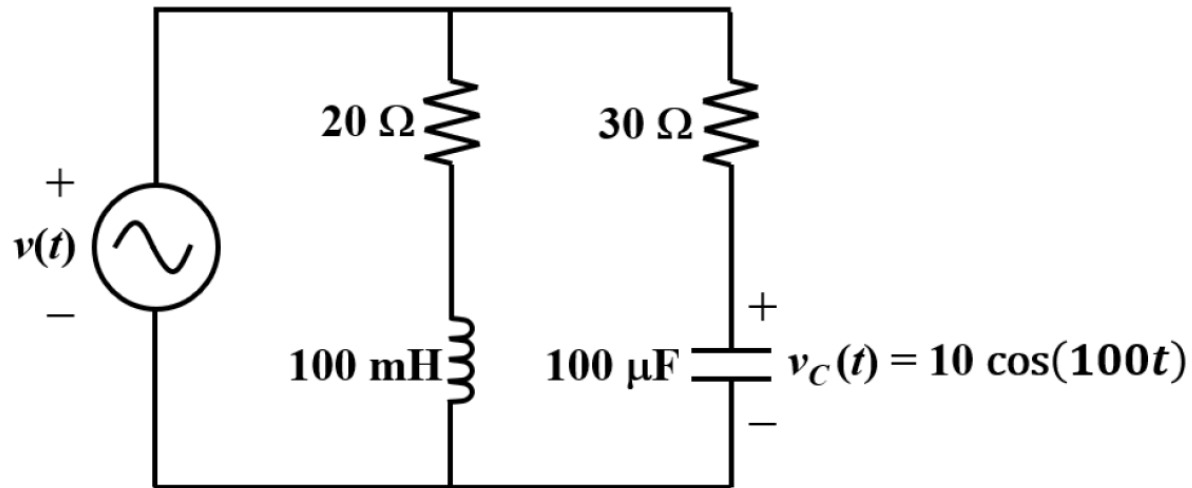


In the circuit shown in the figure above, the voltage $v(t)$ is

- (A) $9.58 \cos(100t - 16.7^\circ)\text{ V}$
- (B) $9.58 \cos(100t + 16.7^\circ)\text{ V}$
- (C) $10.4 \cos(100t + 16.7^\circ)\text{ V}$
- (D) $10.4 \cos(100t - 16.7^\circ)\text{ V}$

Ans: C

Q28

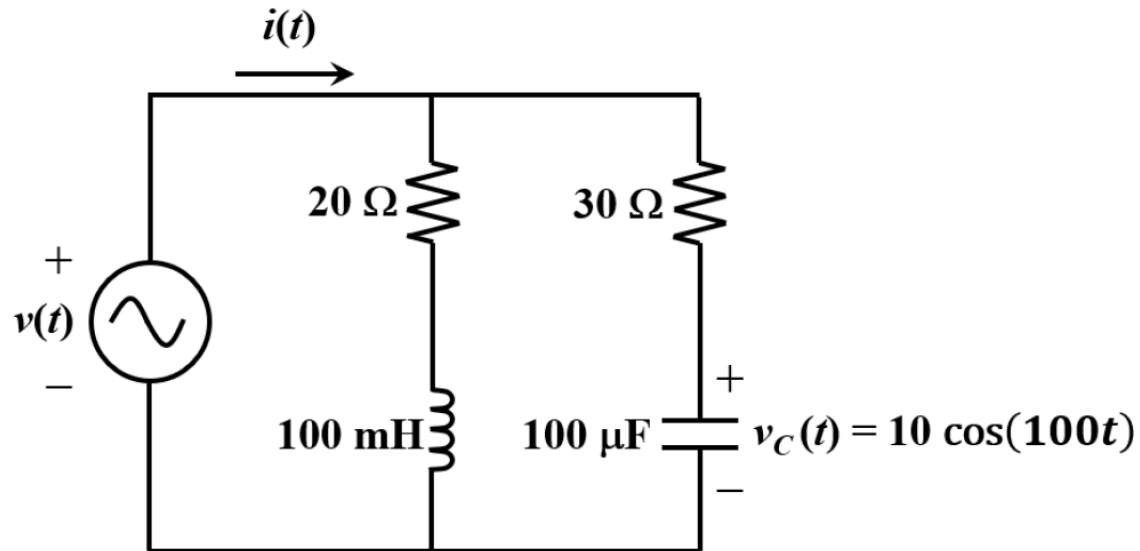


In the circuit shown in the figure above, the current $i(t)$ is

- (A) $237 \cos(100t + 30.9^\circ)\text{ A}$
- (B) $2.17 \cos(100t - 2.5^\circ)\text{ A}$
- (C) $0.46 \cos(100t + 2.5^\circ)\text{ A}$
- (D) $0.54 \cos(100t - 17.6^\circ)\text{ A}$

Ans: C

Q29

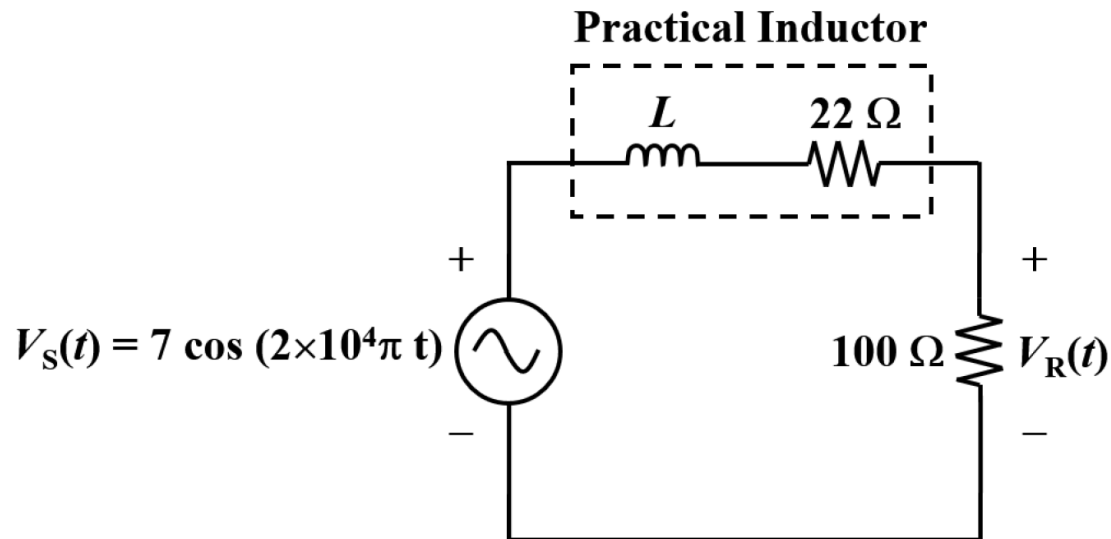


In the circuit shown in the figure above, a 100Ω resistor is connected in series with a practical inductor. The practical inductor has a resistance of 22Ω , and an unknown inductance L . Suppose the phase angle of the voltage $V_R(t)$ is found to be -67° with respect to the source voltage $V_s(t)$, the inductance L can be obtained as:

- (A) 0.825 mH
- (B) 3.75 mH
- (C) 4.57 mH
- (D) 5.88 mH

Ans: C

Q30

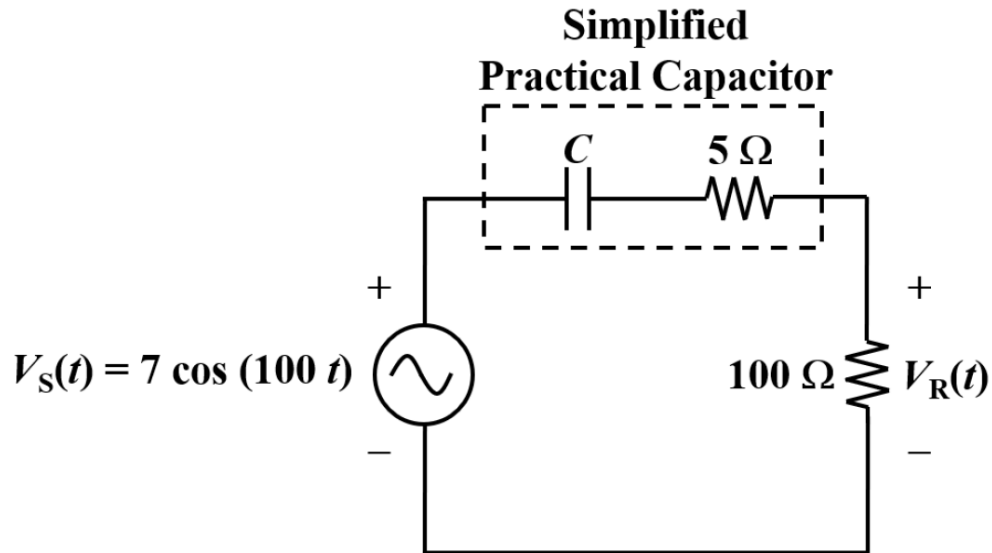

In the circuit shown in the figure above, a $100\ \Omega$ resistor is connected in series with a practical capacitor. The practical capacitor has a series resistance of $5\ \Omega$, and an unknown capacitance C . Suppose the phase angle of the voltage $V_R(t)$ is found to be 43.6° with respect to the source voltage $V_S(t)$, the capacitance C can be obtained as:

- (A) $10\ \mu\text{F}$
- (B) $100\ \mu\text{F}$
- (C) $1\ \text{mF}$
- (D) $10\ \text{mF}$

Ans: B